

Lab 4: FPGA-based Mental Binary Math Game

(ECE6370)

Raj Pramod Dasadia

1. Introduction:

The game, mental binary math is a great way to have fun with math. It's a competitive game in which player's binary and decimal math is tested.

Before the game begins, Authentication of a player is done by entering the last 4 digits of their ID,

Each digit is entered at a time with a fixed set of 4 bit toggle-switches. Every time a digit's binary value is toggled, a load password switch is to be pressed, the process is repeated for all the 4 digits.

Once the authentication is done, a green LED glows. If the authentication is not done, the red LED is on the game will not start and the players will not be able to load their inputs in their corresponding 7 segment until the authentication is done.

After the authentication is done, a timer value needs to be set , since it is a two digit decimal counter, 8 toggle switches are used to set the timer. Once the timer is set Player has to press the Game start button one more time to load the timer value. The next game start button push begins the game. Once the timer starts counting down, RNG button is pressed to generate a random value

Now Player has to analyze the decimal value of that hexadecimal number displayed and then guess a number so that the sum is 15 and then guess the binary equivalent of that number and switch player's set of 4 bit toggle switches and then press load button of to load a valid hexadecimal number to make the sum '15' and display the sum. If the challenge is completed successfully by the player, a green light is turned on, and the red light switches off.

2. Top Module Architecture

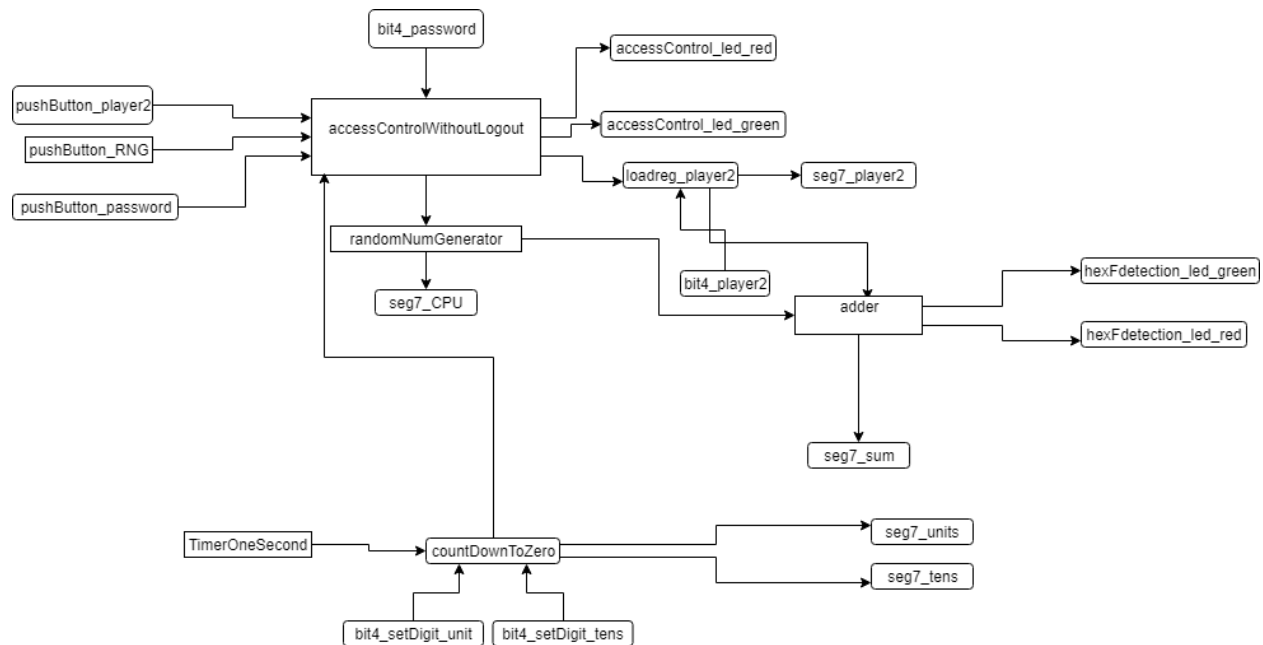


Figure 1

The figure 1 above is the schematic of the top module of lab 2. It connects or wires different independent modules having independent functionalities to produce desired output.

The different modules used here are

- accessControllerwithoutLogout
- counter and randomNumGenerator (counter instantiated in the randomNumGenerator)
- countdownToZero which instantiates modules – Timer1ms, countTo100, countTo10, Timer100ms, TimerOneSecond
- loadReg
- singlePulseButton
- Seg7decoderDisplay
- winDetector
- adder

2.1 AccessControlWithoutlogOut

1. Functionality:

Access Control provides authentication and security. Access controller is designed to accept 4 decimal digits (each 4 bit) one at a time, and checks the entered digits with the authenticated passcode of 4 decimal digits. If the passcode is correct, the push button from the external side is connected to the load register inside the module, thus providing the user an access to the actual functionality of the system. The push button from the external side is always set to 0, thereby providing no access to the user for the actual functionality of the system (Game). Actual access to the Push button to load Player's toggle switch input and RNG button is only provided when The game is in game start mode.

The code is entered in the following fashion.

The first digit is entered by switching the specific set of 4 bit toggle switches. As the first digit is entered, a load button is pushed to load the first digit in the module.

Similarly all the remaining 3 digits are entered and when all the digits match the password saved in the module, access to the load register is granted to the push button signal, thereby allowing the user to operate. As an indication a Green LED glows.

If the password entered is incorrect, the user needs to enter the correct password again, in all the other times, the push button signal is zero and user is not granted an access. Red LED glows all the other times.

Once the password is authenticated the timer for the game is to be set, this is done by using the 8 toggle switches dedicated for the game timer and once both the digit of the timer are set, push button for password is pressed again and the game enters in the game begin stage. Only in this stage the access control provides an access to the RNG and the pushLoad button for player 2's toggled 4 bit input

2. Module design

2.1 One-Procedure Finite state Machine

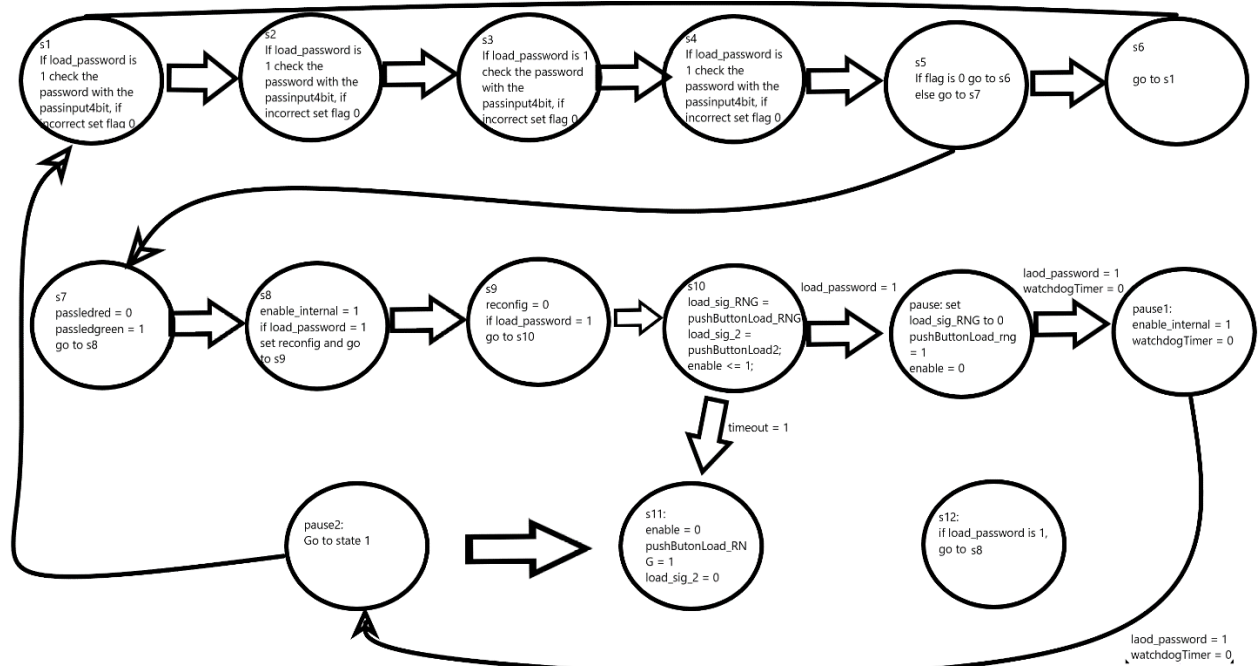


Figure 2

2.1.1 Finite state machine

In figure 1, all the states and the functionality at each state is shown. Before entering the first state, the module is initialized by setting the value of load signal to the load_reg to 0 and the RNGPushButton as 1 so that in any case the user is not granted any access to the game or to load the numbers in the sum module until the state s10 which is the game begin stage.

State 1, State 2, State 3, State 4: if load_password signal is high, every 4 bit decimal input is checked in each stage, if the bit matches with the predefined digit, flag is not changed else flag is set to 0.

State 5: flag is compared, if it is 0, it is sent to stage 6 else it is sent to stage 7.

State 6: Unconditionally transitioned to state 1.

State 7: Unconditionally transitioned to state 8 which is the set timer state. Green LED for authentication is turned on and the red LED is turned off.

If the load_password button is pressed again, game moves to the next state.

State 8: Set reconfig so that timer value can be initialized. If load_password is 1 go to state 9

State 9: If load_password(game begin button) is 1 go to state 10.

State 10: If timeOut is 1, go to State 11 or if load_password = 1, go to Pause.

Pause: if load_password = 1 and watchdogtimer = 0 go to pause 1, else go to state 9.

Pause1: if load_password = 1 and watchdogtimer = 0 go to pause 2 state else go to state 8.

Pause2: Unconditionally go to state 1.

State 11: Set RNG to 1 and load_sig_2 = 0 so that the player can no longer toggle and input their input or use the RNG button. If load_password = 1, go to state 12(game over).

State 12: If load_password is 1, go to State 8.

2.2 accessControl design:

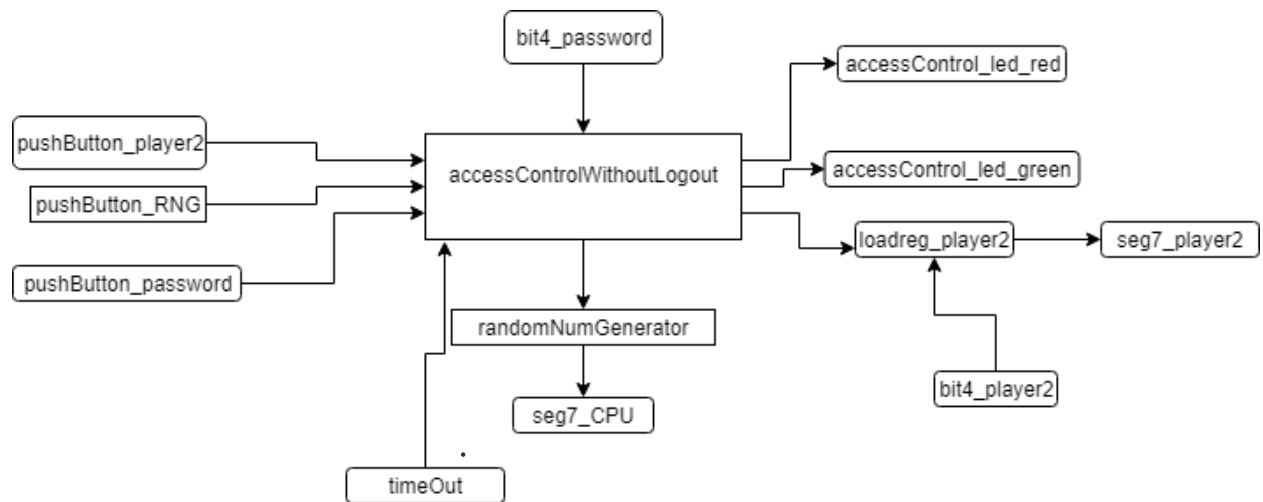


Figure 3

3. Random Number Generator

Functionality: A Random number Generator is used to make the player compete with some random value generated by the processor.

This module makes use of a counter which starts counting the moment begin_count signal is set by the RNG module. It counts at every clock cycle and reinitializes when the value is hex F.

The module provides with an Output of Count whenever the button is released.

Since it counts every clock cycle, it counts upto 50,000,000 times a second and can be called as a true random generator

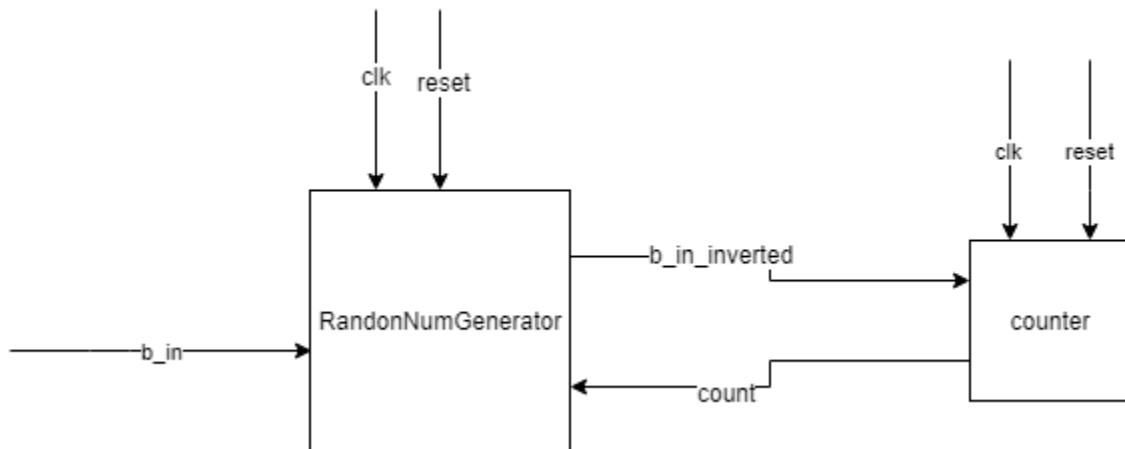


Figure 4

Signals

Input:

B_in: Unshaped button from the Board

B_in_inverted: unverted unshaped button

Output:

Count: counter value that counts upto hex F and reinitializes every clock cycle.

3.1 Simulation

 


Figure 5

It can be observed from the above simulation that when the button is pressed, the RNG module generates a random value by incrementing the value of the counter every second.

The counter reinitializes at every 15th count since we are counting until hex F. Since the value of the timer increments every second, the user has no control over the count and thus it can be considered as a true random number generator.

4. CountdownToZero:

This module instantiates a hierarchy of instantiated modules

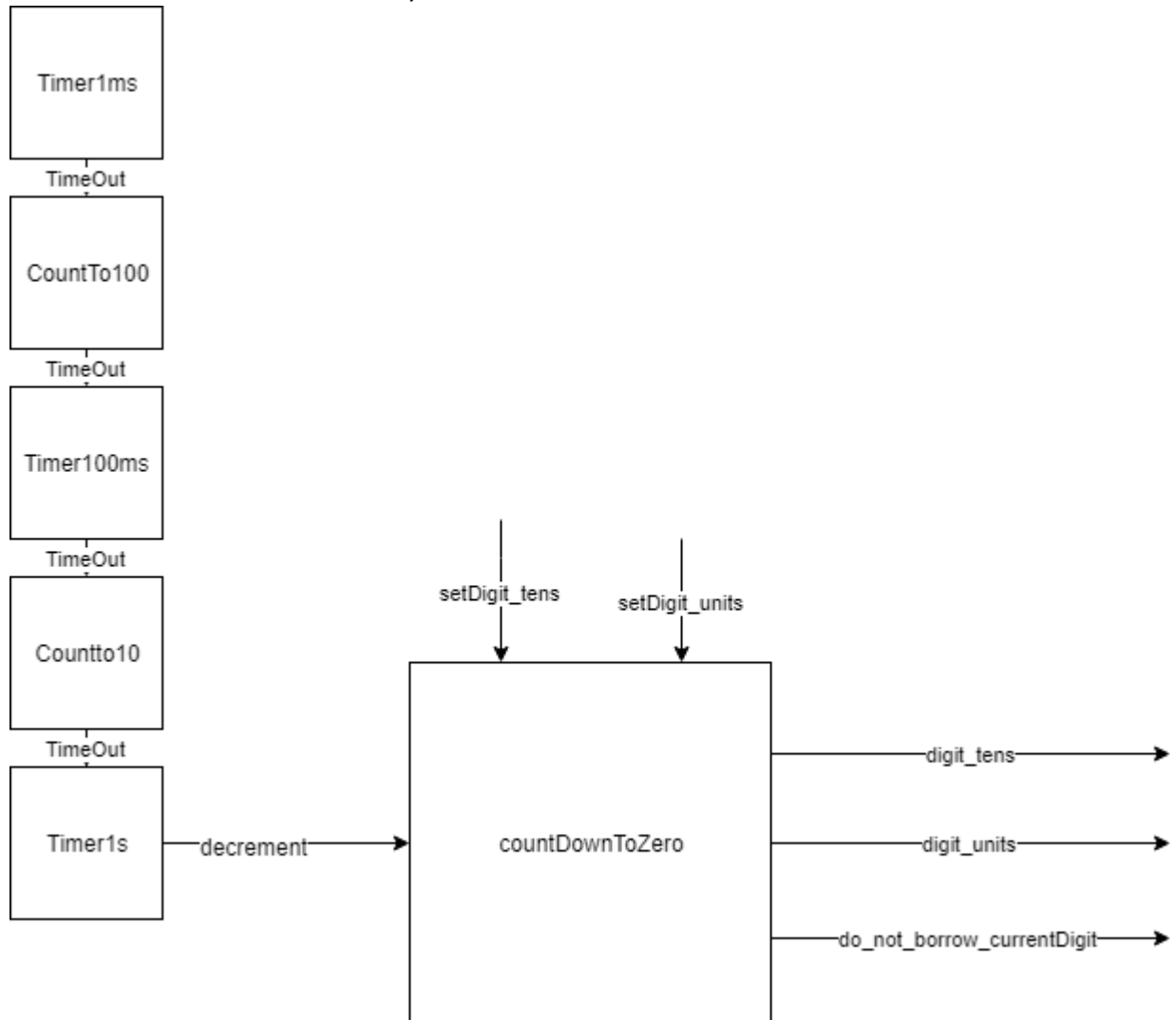


Figure 6

The first module counts by 1 every cycle in a register and reinitializes the register at every 50,000th count and sends out a timeout pulse. Since the clock is 50Mhz, every 50,000th count is actually one milli second.

The output is supplied to other module which counts upto 100 every enable signal. This module is initialized by 100msTimer, so it sends a timeOut pulse every 100th millisecond.

The timeOut of Timer100ms is supplied to Count to 10 which sends an enable at every 10th count.

This module is instantiated by Timer1ms so the TimeOut pulse from this module is sent every 1 second.

This timeOut pulse is inputted to a timer module which is instantiated twice in countdownToZero.

The following is the Schematic the timer module instantiated twice by countDownTozero module

 


Figure 7

in TimerUnits, Timer1s sends decrement pulse every 1s. From the TimerUnits module, every time the digit reaches a value 0, a borrow signal is sent. The timerTens works on on the same logic. Whenever the value of the timerUnits is 0, the do_not_borrow_nextDigit is checked, if it is 0, a borrow signal is set and the digit in TimerUnits is set 9. Same logic is used in TimerTens with the decrement signal acting as borrow for TimerTens.

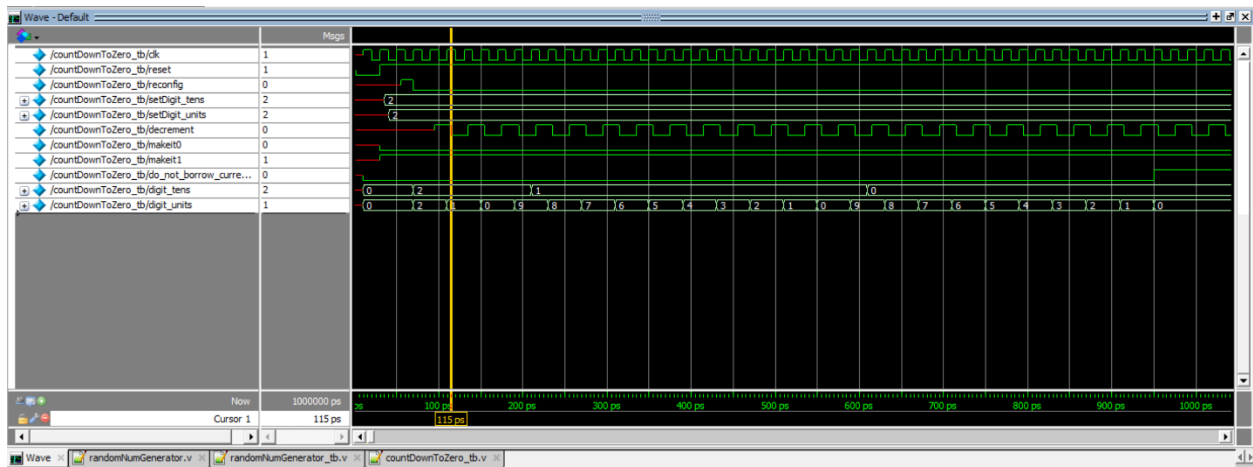


Figure 8

5. Loadreg

Module function: This module has two main functions,

The first function is the reset function, whenever reset is triggered(value is 1), the output of the module should be resetted to a default value of 0. When the value of the reset is 0, The other function comes into action. The other function is load, if the value of load is 0, the output should not change despite of any change in the input. The output of the previous case is stored in the register and it keeps displaying that. When the value of load is 1, the output is set the value of the latest input as the at the rising edge of the clock.

5.1 Module design

 


Figure 9



Figure 10

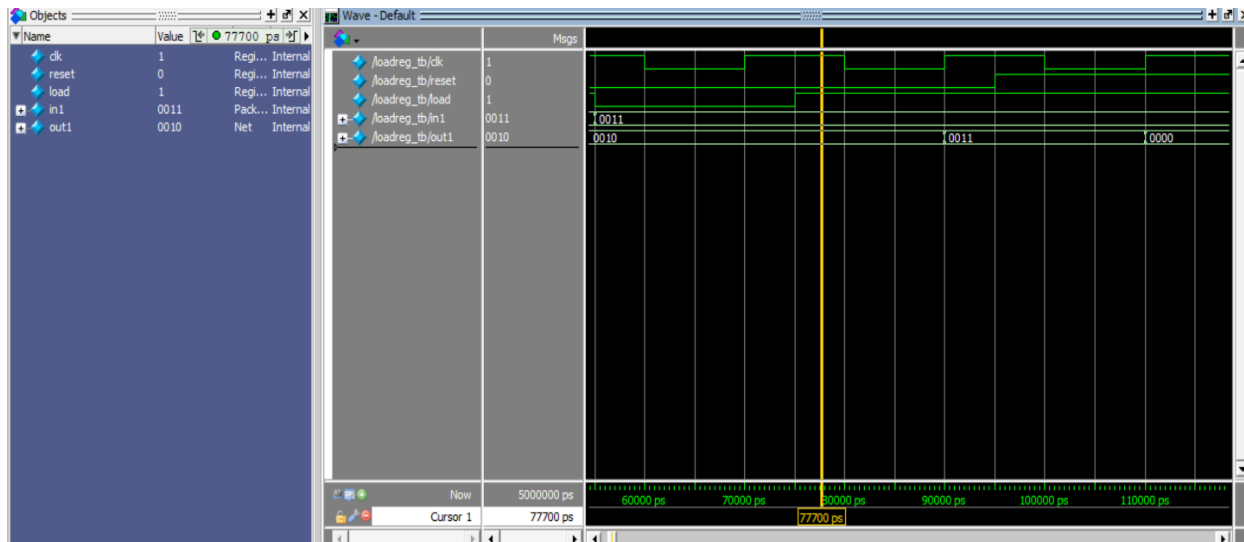


Figure 11

5.2 Simulation conclusion

we can observe that until reset is 1, the output value is 0, as the reset goes to 0, the next control signal for the output is load signal.

It can be seen in the figure 2 that although the value of input is changed, output remains zero until the load is set to 1. When the load is set to 1, the output takes the value of the input at the next rising edge of the clock. So the output becomes 2 at the next rising edge of the clock. Again it is seen that although fourBitIn is set to 3, fourBitOut is not set to 3 until the load is set to 1. After it is set to 1, in the very next cycle's rising edge, fourBitOut is set to 3.


In figure 3 it is observed that again reset is set to 1 and despite of any value of load or fourBitIn, the value of fourBitOut goes to 0 at the very next rising edge of the clock cycle.

6. Button Shaper

1. Functionality:

The function of this module singlePulseButton is to generate a single output pulse whenever a button (active low) is pressed once. In a general case, whenever a button is pressed, it generates an output signal for as long as the button is pressed. For a high frequency clock, even if the button is pressed for a second, it generates a high output for around a million clock cycles. As a solution to this problem we implement this module. This kind of module is specifically used in sensitive applications where generating a single pulse is the most important criteria.

To implement this module we make a 3 stage finite state machine.

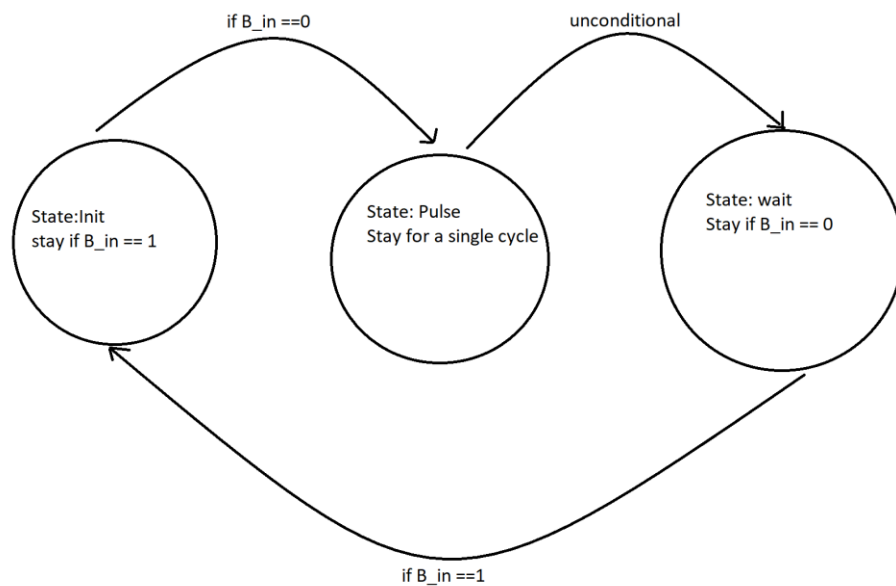*Figure 12*

In the above state cycle it can be seen that when the button is not pressed i.e. B=1 (active low), the output remains zero.

As the button is pressed, i.e. b=0, the output is high for a single cycle since all the instructions are executed in a cycle, and then it unconditionally moves to the next state which is the wait state.

Now, the output remains zero in the wait state even though the button is continuously pressed. As the user releases the button, i.e. B=1, it goes into initial state until the button is pressed again.

6.2 Button Shaper Design analysis

As seen in figure 2, the module has a single bit input and a clock input. The module can be further classified into two modules. Combinational logic, which uses the inputs and produces the output based on the given specific logic. The other module is a state register which maintains the states of the main module. The different states are `s_init`, `s_pulse`, `s_wait`.

`S_init`: As given above is the initial state, and every program starts with initial state since it resets before it starts. It stays in the reset state until the button is pressed.

`S_pulse`: the module stays in this state just for a single cycle and produces an output of 1 and then arrives unconditionally at the wait state.

`S_wait`. The program stays in this state until the button is continuously pressed and when it is released, the program again arrives in the initial state.

Figure 13

Signals:

1. `B_in`: 1 bit input signal indicating the status of the button.
2. State/ nextState: 2 bit registers, storing the value of the defined parameters, `s_init = 0`, `s_pulse = 1`, `s_wait = 2`
3. Pulse: single bit output.

 


Figure 14

As seen in figure 3, initially the reset signal (rst) is low, and the system is resetted and the program is in initial state. The reset is released but the program stays in the initial state until the button is pressed. As the button is pressed, in the next rising edge of the cycle, pulse is 1 just for a single cycle.

The pulse gets low in the next cycle and the program is now in the wait state until the button is released and then the program goes into initial state again.

Simulation Conclusion:

It can be observed from the above figures that only when the button is pressed, we get a single cycle pulse, no matter how long the button is pressed again, the output remains zero after a single pulse. In order to generate another pulse, one has to press the button again.

7. Seven Segment Display

7.1 Functionality:

- i. sevenSegDisplayDecoder: The function of this module is to convert the 4 bit hexadecimal input to a seven bit signal that corresponds to different segments of the display in such a way that the signal leads to the readable character in hexadecimal which is same as the 4 bit hexadecimal that is inputted.
So each of the 4 bit hexadecimal character 0,1,2,3,4,5,6,7,8,9,A,B,C,D,E,F corresponds to 7 bit output signal displaying the same readable hexadecimal character.
- ii. sevenSegDisplayDecoder.tlb: This module is a testbench to test the above module's working. In this module we store each of the 4 bit hexadecimal character in the input register and feed it as an input to the sevenSegDisplayDecoder module with a delay of 10 seconds to obtain the corresponding 7 bit output signal.

7.2 Block Diagram

 


Figure 15

7.3 Simulation

 


Figure 16



Figure 17

 


Figure 18

 


Figure 19

7.4 Result : As seen in figure 2,3,4,5 for each 4 bit hexadecimal input, we get a 7 bit output signal which generates readable same hexadecimal character in the 7 segment display. Note that the signal to turn on a segment is '0' and the signal required to turn off a segment is '1' due to current sinking property. Each hexadecimal has it's unique set of 7 bits output signal.

8. adder

This module is a simple combinational module that accepts two 4 bit input and produces a sum of 4 bit output.

The max number that the adder can sum upto is a hex F, since the output is only 4 bits.



Figure 20

9. Video Demonstration

In the video, user authentication is demonstrated followed by examining edge cases. This is followed by testing of Pause feature, Resume feature, Timer reset feature, and Log out state. It also demonstrates working of RNG. This is followed by the timeout test where once the timer value is 0, player cannot access the game.

https://drive.google.com/file/d/1wHnB1C-RH695On3yr2_KbWsAksJ2e5Bg/view?usp=sharing

The second feature tests RNG and player load button, it also tests win detection which are the main feature of the game.

<https://drive.google.com/file/d/1d704rGhWAFcy7wKIJbCNiBoDjpzsAyVL/view?usp=sharing>

10. Conclusion

All the modules above have been tested individually and incorporated in the project and tested for their functionality in the project. All the functionality and the edge cases have been tested and works as expected in the project

Appendix

```
//4014
```

```
//testLED1, testLED2, testLED3, testLED4, testLED5 are just to test the states
```

```
module accessControlWithLogout (clk, reset, load_sig_RNG, load_sig_2, load_password,
pushButtonLoad_RNG, pushButtonLoad2, passinput4bit, timeout, reconfig, enable, passredled,
passgreenled, testLED1, testLED2, testLED3, testLED4, testLED5);
```

```
input clk, reset;
input load_password;    //signal from button shaper
input [3:0] passinput4bit;
input pushButtonLoad_RNG, pushButtonLoad2 ; //signal from button shaper
input timeout;
```

```
reg flag;
reg [3:0] state;
output load_sig_RNG, load_sig_2; //signal to the load register
output passredled, passgreenled;
output reconfig, enable;
reg reconfig, enable;
reg passredled, passgreenled;
reg load_sig_RNG, load_sig_2 ;
output reg testLED1, testLED2, testLED3, testLED4, testLED5;
```

```
parameter s1 = 0, s2 = 1, s3 = 2, s4 = 3, s5 = 4, s6 = 5, s7 = 6, s8 = 7, s9 = 8, s10 = 9, s11 = 10, s12
= 11;
```

```
always @ (posedge clk)
```

```
begin
```

```
if (reset == 0)
begin
    flag <= 1;
    load_sig_RNG <= 1;
    load_sig_2 <= 0;
    passredled <= 1;
    passgreenled <= 0;
    state <= s1;
end
else
begin
    case (state)

s1:
    begin
        if (load_password == 1)
        begin
            if (passinput4bit == 4'b0100)
                begin
                    state <= s2;
                end
            else
                begin
                    flag <= 0;
                    state <= s2;
                end
            end
        end
        else
        begin
            state <= s1;
        end
    end

s2:
    begin
        if (load_password == 1)
        begin
            if (passinput4bit == 4'b0000)
                begin
                    state <= s3;
                end
            else
                begin
                    flag <= 0;
                end
            end
        end
    end
end
end
```

```
        state <= s3;
    end
end
    else
    begin
        state <= s2;
    end
end

s3:
begin
    if (load_password == 1)
    begin
        if ( passinput4bit == 4'b0001)
        begin
            state <= s4;
        end
        else
        begin
            flag <= 0;
            state <= s4;
        end
    end
    else
    begin
        state <= s3;
    end
end

s4:
begin
    if (load_password == 1)
    begin
        if ( passinput4bit == 4'b0100)
        begin
            state <= s5;
        end
        else
        begin
            flag <= 0;
            state <= s5;
        end
    end
    else
    end
```

```
        begin
            state <= s4;
        end
    end

s5:
begin
    if (flag == 0)           //password incorrect
    begin
        state <= s6;
    end
    else
        begin
            state <= s7;           //password correct
        end
    end
end

s6:
begin
    flag <= 1;
    state <= s1;
end

s7:
begin
    passgreenled <= 1;
    passredled <= 0;
    state <= s8;
end

s8:
begin
    testLED1 <= 1;
    testLED5 <= 0;
    if(load_password == 0)
        begin
            state <= s8;
            reconfig <= 0;
        end
    else
        begin
```

```

        reconfig <= 1;
        state <= s9;
    end
end

s9:
begin
    testLED1 <= 0; testLED2 <= 1;
    reconfig <= 0;
    if(load_password == 0)
        begin
            state <= s9;
        end
    else
        begin
            state <= s10;
        end
    end
end

s10:
begin
    testLED2 <= 0; testLED3 <= 1;
    load_sig_RNG <= pushButtonLoad_RNG;           //the push button
    from rng is equal to count begin
        load_sig_2 <= pushButtonLoad2;
        enable <= 1;
        if(timeout == 1)
            begin
                state <= s11;
            end
        else
            begin
                state <= s10;
            end
        end
    end
end

s11:
begin
    testLED3 <= 0; testLED4 <= 1;
    enable <= 0;
    load_sig_RNG <= 1;
    load_sig_2 <= 0;
    if (load_password <= 0)
        begin

```



```

                                state <= s11;
                                end
                                else
                                    begin
                                        state <= s12;
                                    end
                                end
                            end

                            s12:
                            begin
                                testLED4 <= 0; testLED5 <= 1;
                                if (load_password <= 0)
                                    begin
                                        state <= s12;
                                    end
                                else
                                    begin
                                        state <= s8;
                                    end
                                end
                            end
                        default:
                        begin
                            state <= s1;
                        end
                    endcase
                end
            end
        endmodule

//4014
module countDownToZero(clk, reset, reconfig, setDigit_tens, setDigit_units, decrement,
do_not_borrow_currentDigit, digit_tens, digit_units);//, makeit0, makeit1);
input clk, reset;
input reconfig;
input decrement;
input [3:0] setDigit_units;
input [3:0] setDigit_tens;
//input makeit0, makeit1;
output do_not_borrow_currentDigit;
output [3:0] digit_units;
output [3:0] digit_tens;
wire borrow;
wire do_not_borrow;
//parameter makeit0 = 0, makeit1 = 1;

```

```

wire makeit1 ;
assign makeit1 = 1'b1;
wire makeit0;
timer TimerTens(clk, reset, reconfig, setDigit_tens, borrow, makeit1, do_not_borrow, makeit0,
digit_tens);
timer TimerUnits(clk, reset, reconfig, setDigit_units, decrement, do_not_borrow,
do_not_borrow_currentDigit, borrow, digit_units);

endmodule
//Author 4014
//counter module for rng

```

```

module counter( clk, reset, begin_count, count);
input clk, reset;
input begin_count;
output [3:0] count;
reg [3:0] count;

```

```

always @ (posedge clk)
begin
    if (reset == 0)
        begin
            count <= 0;
        end

    else if((count == 15) | (count > 15))
        begin
            count <= 0;
        end
    else
        begin
            begin
                if (begin_count == 1 )
                    begin
                        count <= count + 1;
                    end
            end
        end
    end
end
endmodule

```

```
//Author 4014
//count to 10 module for 1ms module

module CountTo10(clk, reset, count, timeOut);
input clk, reset;
input count;
output timeOut;
reg timeOut;
reg [0:3] counter;
always @ (posedge clk)
begin

    if (reset == 0)
    begin
        timeOut <= 0;
        counter <= 0;
    end

    else
    begin
        if(count == 0)
            begin
                counter <= counter;
                timeOut <= 0;
            end
        else
            begin
                if(counter >10)
                    begin
                        counter<=0;
                    end
                else if(counter == 10)
                    begin
                        counter <= 0;
                        timeOut <= 1;
                    end
                else
                    begin
                        timeOut <= 0;
                        counter <= counter + 1;
                    end
            end
        end
    end
end
```

```

        end
    end
end
endmodule

```

```

//Author 4014
//Count to 100 for 1 ms module
module CountTo100(clk, reset, count, timeOut);
input clk, reset;
input count;
output timeOut;
reg timeOut;
reg [0:6] counter;
always @ (posedge clk)
begin

    if (reset == 0)
    begin
        timeOut <= 0;
        counter <= 0;
    end

    else
    begin
        if(count == 0)
            begin
                counter <= counter;
                timeOut <= 0;
            end
        else
            begin
                if(counter >100)
                    begin
                        counter<=0;
                    end
                else if(counter == 100)
                    begin
                        counter <= 0;
                        timeOut <= 1;
                    end
                else
                    begin

```

```
endmodule
```

```
// 6370
// Homework 2
// Author: Raj Pramod Dasadia, 4014
// Adds two 4 bit numbers
module fourBitAdder (in1, in2, sum);

    input [3:0] in1, in2;
    output [3:0] sum;
    reg [3:0] sum;

    always @ (in1, in2)
        begin

            sum = in1 + in2;

        end
endmodule
```

```
// 6370
// Homework 2
// Author: Raj Pramod Dasadia, 4014
// detects if the input is a binary 1111
module hexFdetector (hex_in, out_sigRed, out_sigGreen);

input [3:0] hex_in;
output out_sigRed, out_sigGreen;

reg out_sigRed, out_sigGreen;

    always @ (hex_in)
        if (hex_in == 4'b1111)
            begin
                out_sigGreen = 1; out_sigRed = 0;
            end
        else
            out_sigRed = 1; out_sigGreen = 0;
    end
```

```

        end
    else
        begin
            out_sigRed = 1; out_sigGreen = 0;
        end
    end

endmodule

// Lab 6
// Author: Raj Pramod Dasadia, 4014
// Top module to connect all the modules

module LAB3_DASADIA_R ( clk, reset, bit4_player2, bit4_password, bit4_setDigit_units,
bit4_setDigit_tens, pushButton_RNG, pushButton_player2, pushButton_password,
                        seg7_CPU, seg7_player2, seg7_sum, seg7_units, seg7_tens,
hexFddetection_led_red, hexFddetection_led_green, accessControl_led_red,
accessControl_led_green, testLED1, testLED2, testLED3, testLED4, testLED5);

input clk, reset;

input pushButton_RNG, pushButton_player2, pushButton_password;

input [3:0] bit4_player2, bit4_password;
input [3:0] bit4_setDigit_tens, bit4_setDigit_units;

output hexFddetection_led_red, hexFddetection_led_green, accessControl_led_red,
accessControl_led_green;

output [6:0] seg7_CPU, seg7_player2, seg7_sum, seg7_units, seg7_tens;

wire load_sig_player1, load_sig_player2, pulse_player2, pulse_password;
wire [3:0] fourBitOut_player2, sum4bit, digit_tens, digit_units, count ;
wire load_sig_RNG, reconfig, decrement, enable, timeout;

output testLED1, testLED2, testLED3, testLED4, testLED5;

```

```

accessControlWithLogout accessControlWithLogout1 (clk, reset, load_sig_RNG,
load_sig_player2, pulse_password, pushButton_RNG, pulse_player2, bit4_password, timeout,
reconfig, enable, accessControl_led_red, accessControl_led_green, testLED1, testLED2,
testLED3, testLED4, testLED5);

randomNumGenerator randomNumGenerator1 (clk, reset, load_sig_RNG, count);

fourBitAdder adder (count, fourBitOut_player2, sum4bit);

hexFdetector win_detector (sum4bit, hexFdetector_led_red, hexFdetector_led_green);

loadreg loadreg_player2 ( clk, reset, load_sig_player2, bit4_player2, fourBitOut_player2 );

sevenSegDisplayDecoder sevenSegDisplayDecoder_CPU (count, seg7_CPU);
sevenSegDisplayDecoder sevenSegDisplayDecoder_player2 (fourBitOut_player2, seg7_player2);
sevenSegDisplayDecoder sevenSegDisplayDecoder_sum (sum4bit, seg7_sum);
sevenSegDisplayDecoder sevenSegDisplayDecoder_tens (digit_tens, seg7_tens);
sevenSegDisplayDecoder sevenSegDisplayDecoder_units (digit_units, seg7_units);

singlePulseButton singlePulseButton_player2 (pushButton_player2, pulse_player2, clk, reset);
singlePulseButton singlePulseButton_password (pushButton_password, pulse_password, clk,
reset);

countDownToZero countDownToZero1(clk, reset, reconfig, bit4_setDigit_tens,
bit4_setDigit_units, decrement, timeout, digit_tens, digit_units);

TimerOneSecond TimerOneSecond1(clk, reset, enable, decrement);

Endmodule

// 6370
// Homework 4
// Author: Raj Pramod Dasadia, 4014
// load register with reset and clock trigger

module loadreg ( clk, reset, load, fourBitIn, fourBitOut );

```

```

input clk, reset, load;
input [3:0] fourBitIn;
output [3:0] fourBitOut;
reg [3:0] fourBitOut;

always @ (posedge clk)

begin
    if ( reset == 1)
        begin
            if ( load == 1)
                begin
                    fourBitOut = fourBitIn;
                end
            end
        else if (reset == 0)
            begin
                fourBitOut = 4'b0000;
            end
        end
end
endmodule

```

```

//Author 4014
//rng module instantiating counter module
module randomNumGenerator (clk, reset, b_in, count);
input clk, reset;
input b_in;
output [3:0] count;
assign b_in_inverted = ~b_in;

counter rng_counter (clk, reset, b_in_inverted, count);

endmodule

```

```

// 6370
// Homework 2

```



```
// Author: Raj Pramod Dasadia, 4014
// Displays 4 bit binary into 7 segment display device
module sevenSegDisplayDecoder (fourbit_in, sevenbit_out);

input [3:0] fourbit_in;
output [6:0] sevenbit_out;
reg [6:0] sevenbit_out;

    always @ (fourbit_in)
        begin
            case (fourbit_in)
                4'b0000:
                    begin
                        sevenbit_out = 7'b1000000;
                    end
                4'b0001:
                    begin
                        sevenbit_out = 7'b1001111;
                    end
                4'b0010:
                    begin
                        sevenbit_out = 7'b0100100;
                    end
                4'b0011:
                    begin
                        sevenbit_out = 7'b0110000;
                    end
                4'b0100:
                    begin
                        sevenbit_out = 7'b0011001;
                    end
                4'b0101:
                    begin
                        sevenbit_out = 7'b0010010;
                    end
                4'b0110:
                    begin
                        sevenbit_out = 7'b0000010;
                    end
                4'b0111:
                    begin
                        sevenbit_out = 7'b1111000;
                    end
                4'b1000:
                    begin
                        sevenbit_out = 7'b1000000;
                    end
            end
        end
    end
```

```
begin
    sevenbit_out = 7'b0000000;
end
4'b1001:
begin
    sevenbit_out = 7'b0010000;
end
4'b1010:
begin
    sevenbit_out = 7'b0001000;
end
4'b1011:
begin
    sevenbit_out = 7'b0000011;
end
4'b1100:
begin
    sevenbit_out = 7'b1000110;
end
4'b1101:
begin
    sevenbit_out = 7'b0100001;
end
4'b1110:
begin
    sevenbit_out = 7'b0000110;
end
4'b1111:
begin
    sevenbit_out = 7'b0001110;
end
default:
begin
    sevenbit_out = 7'b0000000;
end
endcase
end
endmodule
```

```
//Author 4014
```

```
//Button Shaper module
module singlePulseButton (b_in, pulse, clk, rst);

input b_in;
input clk, rst;

output pulse;

reg pulse;
reg [1:0] state, nextState;

parameter s_init = 0, s_pulse = 1, s_wait = 2;

always @ ( state, b_in)

begin

    case (state)

        s_init:
        begin
            pulse = 0;
            if (b_in == 1)
                begin
                    nextState = s_init;
                end
            else
                begin
                    nextState = s_pulse;
                end
            end

        s_pulse:
        begin
            pulse = 1;
            nextState = s_wait;
        end

        s_wait:
        begin
            pulse = 0;
            if (b_in == 0)
                begin
```

```

        nextState = s_wait;
    end
else
    begin
        nextState = s_init;
    end
end

end

default:
    begin
        nextState = s_init;
    end
endcase
end

always @ (posedge clk)
    begin
        if (rst == 0)
            begin
                state <= s_init;
            end
        else
            begin
                state <= nextState;
            end
        end
    end

endmodule

//Author 4014
//Digit clock module
module timer(clk, reset, reconfig, setDigit, decrement, do_not_borrow_nextDigit,
do_not_borrow_currentDigit, borrow, digit);
input clk, reset;
input reconfig;
input [3:0] setDigit;
input decrement;
input do_not_borrow_nextDigit;
output reg do_not_borrow_currentDigit;
output reg borrow;

```

```

output reg [3:0] digit;

always @ (posedge clk)
    begin
        if(reset == 0)
            begin
                do_not_borrow_currentDigit <= 0;
                borrow <= 0;
                digit <= 4'b0000;
            end
        else
            begin
                if(reconfig == 1)
                    begin
                        do_not_borrow_currentDigit <= 0;
                        if(setDigit > 9)
                            begin
                                digit <= 4'b1001;
                            end
                        else
                            begin
                                digit <= setDigit;
                            end
                    end
                else
                    begin
                        if(decrement == 1)
                            begin
                                if(digit == 4'b0000)
                                    begin

                                if(do_not_borrow_nextDigit == 1)
                                    begin

                                //digit <= 4'b0000;

                                do_not_borrow_currentDigit <= 1;

                                end
                            end
                        else
                            begin

                                borrow <= 1;

                                digit <= 4'b1001;

```

```

1;

if(do_not_borrow_nextDigit == 1)
begin
    do_not_borrow_currentDigit <= 1;
end

end

else
begin
    borrow <= 0;
    digit <= digit - 1;

    if(digit == 1)
        begin
            borrow <= 1;
            digit <= 0;
        end
    end
end

end

endmodule

```

```
//Author 4014
//1ms module counting upto 50,000
module Timer1ms(clk, reset, enable, timeOut);
input clk, reset;
input enable;
output timeOut;
reg timeOut;
reg [15:0] counter;
```

```
always @ (posedge clk)
begin

    if (reset == 0)
    begin
        timeOut <= 0;
        counter <= 0;
    end

    else
    begin
        if(enable == 0)
        begin
            counter <=0;
            timeOut <=0;
        end

        else
        begin
            if (counter >50000)
            begin
                counter<=0;
            end
            else if(counter == 50000)
            begin
                counter <= 0;
                timeOut <= 1;
            end

            else
            begin
                timeOut <= 0;
                counter <= counter + 1;
            end
        end
    end
end
endmodule
```

```
module Timer100ms(clk, reset, enable, timeOut);  
input clk, reset;  
input enable;  
output timeOut;  
//reg timeOut;  
wire count;  
  
Timer1ms Timer1ms_1(clk, reset, enable, count);  
CountTo100 CountTo100_1(clk, reset, count, timeOut);  
  
endmodule
```

```
//Author 4014  
//timer module instantiating digit counter twice for tens and hundred's place of counter  
module TimerOneSecond(clk, reset, enable, timeOut);  
input clk, reset;  
input enable;  
output timeOut;  
//reg timeOut;  
wire count1;  
  
Timer100ms Timer100ms_2(clk, reset, enable, count1);  
CountTo10 CountTo10_2(clk, reset, count1, timeOut);  
  
endmodule
```

End of Design Document

